

**Pr2. CIRCUIT AND SIMULATION LAB**

Name of the Course: Diploma in Electrical Engineering			
Course code:		Semester	3 <sup>rd</sup>
Total Period:	90	Examination :	3hrs
Lab. periods:	6 P / week	Sessional:	50
Maximum marks:	100	End Semester Examination ::	50

**A. Rationale:**

The response of Electrical Circuit can be verified practically by applying different theorems and fundamental techniques. The students will become sure that the theoretical tricks which they have learned from books are true. The students will become competent in the field of circuit analysis

**B. Objective:**

On completion of the lab course the student will be able to:

1. Verify the theorems using different components.
2. Know the various types of filters.
3. Simulate different circuits using P-Spice/MATLAB software.

**C. Course content in terms of specific objectives:**

1. Measurement of equivalent resistance in series and parallel circuit
2. Measurement of power and power factor using series R-L-C Load.
3. Verification of KCL and KVL.
4. Verification of Super position theorem
5. Verification of Thevenin's Theorem
6. Verification of Norton's Theorem
7. Verification of Maximum power transfer Theorem
8. Determine resonant frequency of series R-L-C circuit.
9. Study of Low pass filter & determination of cut-off frequency
10. Study of High pass filter & determination of cut-off frequency
11. Analyze the charging and discharging of an R-C & R-L circuit with oscilloscope and Compute the time constant from the tabulated data and determine the rise time graphically.
12. Construct the following circuits using P-Spice/MATLAB software and compare the measurements and waveforms.
  - i. Superposition theorem
  - ii. Series Resonant Circuit
  - iii. Transient Response in R-L-C series circuit

**Note:** P-Spice/MATLAB software might be loaded in 10 systems.

## **Aim of the Experiment :-**

Varification of Ohm's law.

## **Apparatus Required :-**

1. C.T. Trainer Kit
2. Patch Cord

## **Theory :-**

**OHM'S LAW :-** This law states that as long as physical conditions remains same. The electric current flowing through a conductor is proportional to the voltage applied across it and is given by :

$$I = V/R$$

Where 'R' is the resistance of the conductor to current flow in ohms.

'V' is the voltage in volts.

'I' is the current in Amperes.

The above expression can be put in different forms as below.


$$V = IR$$

$$R = V/I$$


**Resistance :-** By definition of a conductor is said to have a resistance of one ohm if a voltage of 1 volt applied across its causes a current of 1 amp to flow through the conductor.
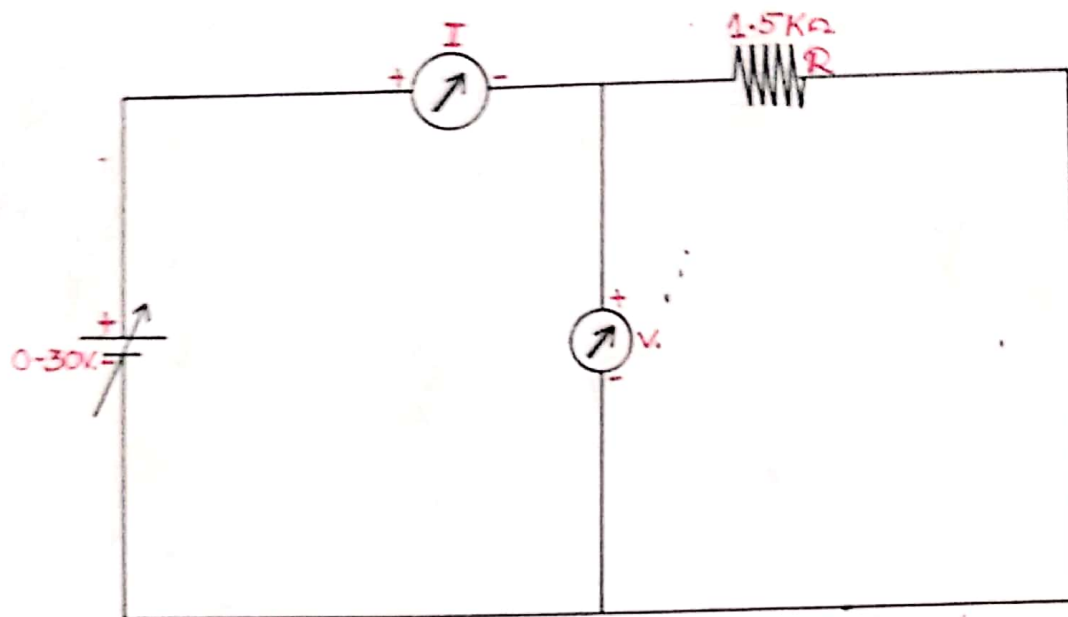
## **Varification of ohms law :-**

Ohm's law can be verified by varying the D.C. voltage applied across a resistor & recording the values of corresponding current. The graph " V " verses " I " is a straight line as shown in fig (B). thus the resistor is a linear component.



CKT. FOR VERIFICATION OF OHM'S LAW

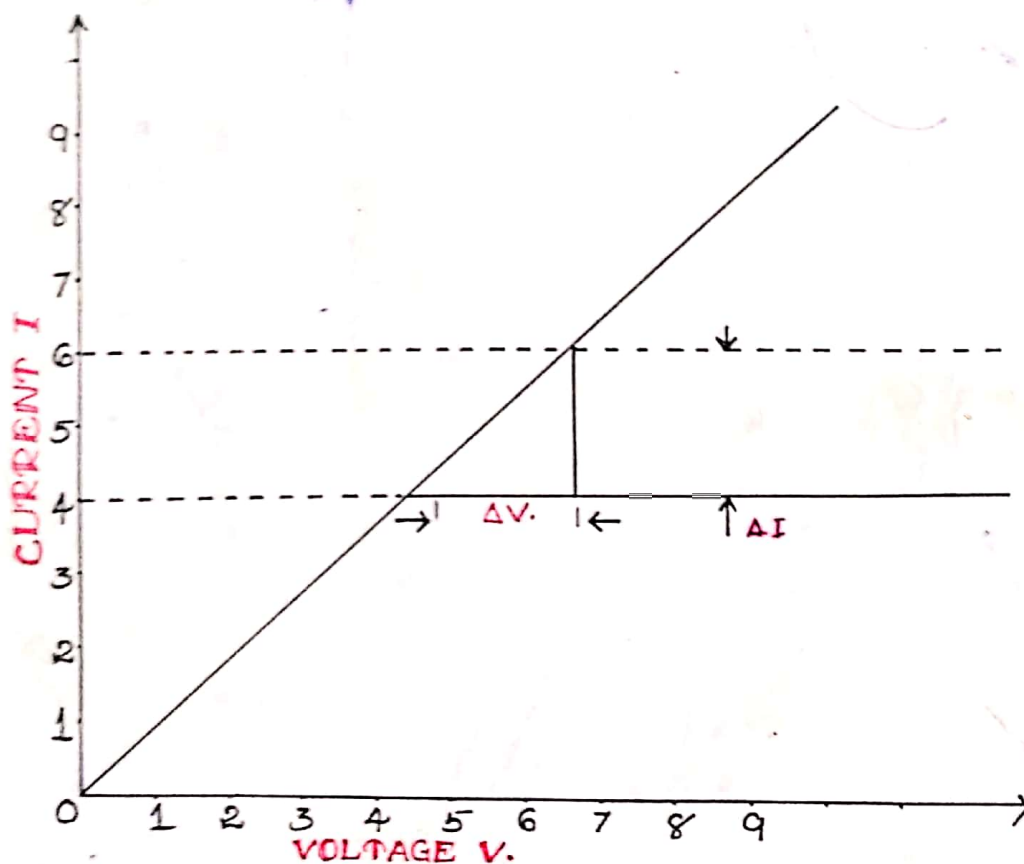

V.I. CHARACTERISTICS VERIFYING OF A RESISTOR OHM'S LAW.



## **Aim of the experiment :-**

Verification of law of resistance in series.

## **Apparatus required :-**

1. Patch Cord
2. C.T. Trainer Kit

## **Theory :-**

A conductor having resistances  $R_1$ ,  $R_2$  &  $R_3$  are connected in series. The equivalent resistance or total resistance between the two terminals is equal to the sum of three individual resistances. Being a series circuit it should be remember that :-

1. Current is the same through all the three conductors.
2. But voltage drop across each is different due to its different resistances given by ohm's law.
3. Sum of the voltage drop is equal to the voltage applied across the three conductors.

$$V = IR$$

$$V = V_1 + V_2 + V_3$$

$$IR = IR_1 + IR_2 + IR_3$$


$R$  equivalent of the series combination

$$R = R_1 + R_2 + R_3$$

## **Characteristics :-**

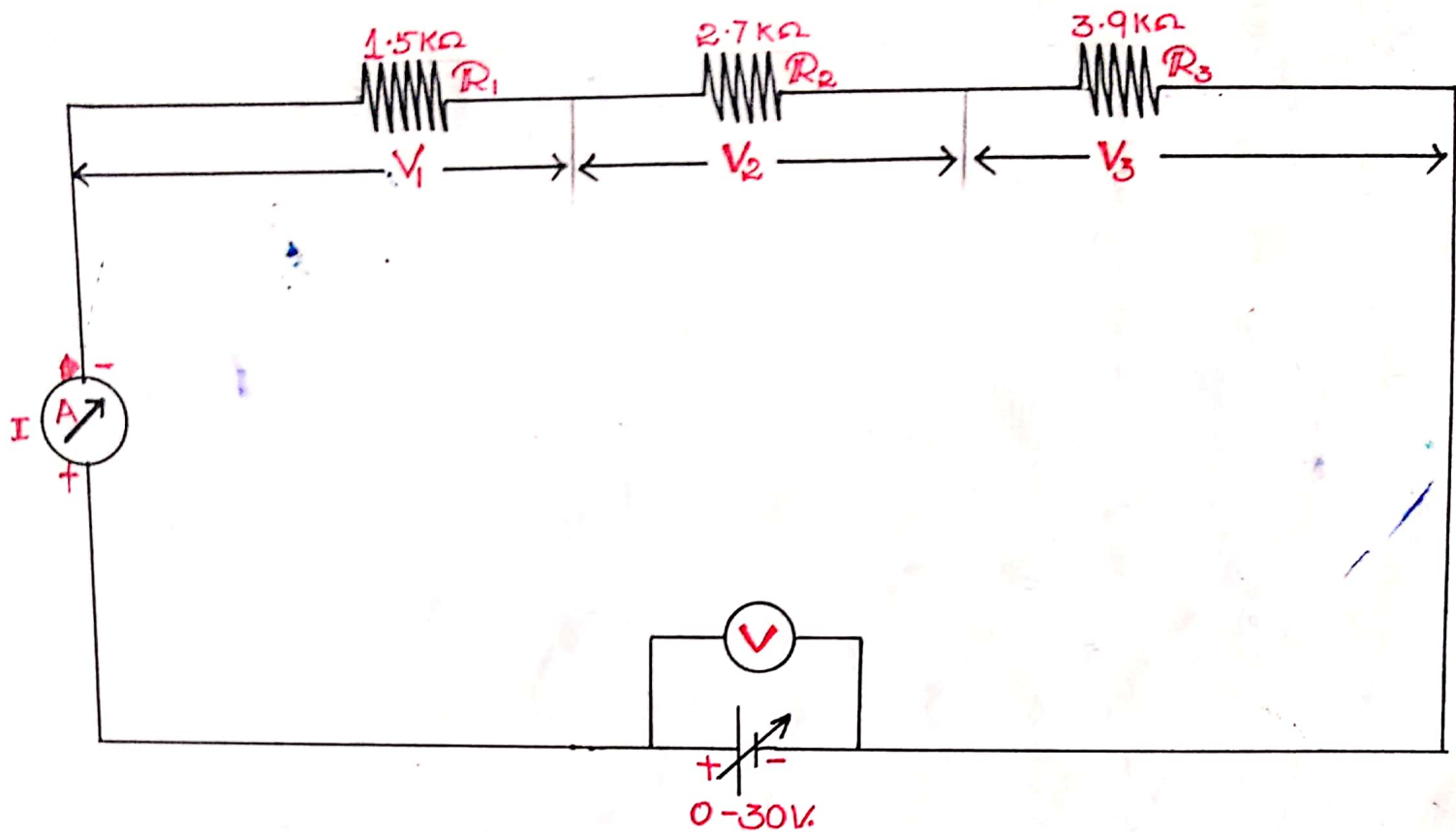1. Same current flows through all parts of the circuit .
2. Different resistors of there individual voltage drop.
3. Voltage drop are additive.
4. Applied voltage equals the sum of different voltage drop.
5. Resistances are additive.
6. Powers are additive.






$R_1 \rightarrow 1.5K\Omega$ ,  $R_2 \rightarrow 2.7K\Omega$ ,  $R_3 \rightarrow 3.9K\Omega$ ,  $V \rightarrow (0-30)V$

Ckt. DIA. OF SERIES RESISTANCE.

### THEORY :-

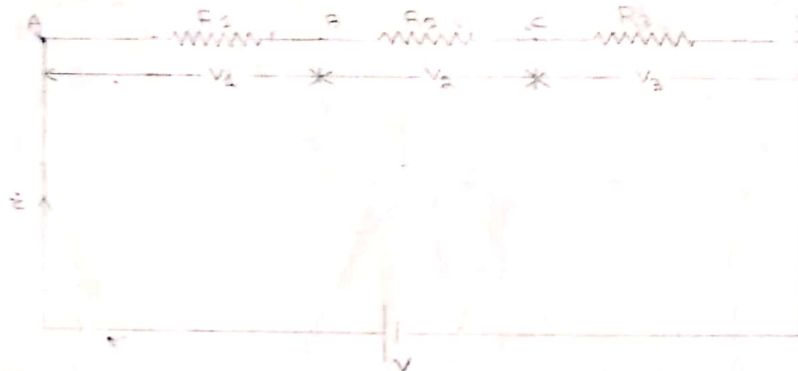

Here taking  $R_1 = 1\text{ k}\Omega$ ,  $R_2 = 2.2\text{ k}\Omega$ ,  $R_3 = 4.7\text{ k}\Omega$

### **Procedure :-**

1. Connect the ammeter, voltmeter, resistor to the source by using patch cord as per the circuit diagram.
2. Check one's more the connection of parameter as per the circuit diagram.
3. Then switch on the supply.
4. Measure the total current  $I$  & source voltage  $V$ .
5. Calculate the value of  $R$  equivalent as  $R_{eq} = V/I$ .
6. Measure  $V_1$ ,  $V_2$ ,  $V_3$  across the resistor  $R_1$ ,  $R_2$  &  $R_3$  respectively.
7. Calculate the value of  $R_1$ ,  $R_2$  &  $R_3$  as  $R_1 = V_1/I$ ,  $R_2 = V_2/I$ ,  $R_3 = V_3/I$ . Find the  $R_{eq}'$  which is equal to  $R_1 + R_2 + R_3$ . Then difference between  $R_{eq}$  &  $R_{eq}'$

### **Tabulation :-**

No	Voltage in Volt	Current in Amp	$R_{eq} = V/I$ in ohm	$V_1$ in volt	$V_2$ in volt	$V_3$ in volt	$R_1 = V_1/I$ in ohm	$R_2 = V_2/I$ in ohm	$R_3 = V_3/I$ in ohm	$R_{eq}'$ in ohm	Difference $R_{eq} - R_{eq}'$

### **Conclusion :-**

From the above experiment we observed the laws of resistances in series is satisfied.

\*\*\*

## **Aim of the Experiment :**

To verification of laws of resistance in parallel.

## **Apparatus Required :-**

1. Patch cord
2. C.T. Trainer kit.

## **Theory :-**

Three resistance are joined as in circuit diagram are said to be connected in parallel. In this case (1) potential difference across all resistances is the same (2). Current in each resistor different and is given by ohm's law. (3) The total current is the sum of three separate currents.

$$I = I_1 + I_2 + I_3 = V/R_1 + V/R_2 + V/R_3$$

Now  $I = V/R$  where  $V$  is the applied voltage.

And  $R =$  Equivalent resistance of the parallel combination.


$$V/R_{eq} = V/R_1 + V/R_2 + V/R_3$$

$$\Rightarrow 1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_3$$

## **Characteristics :-**

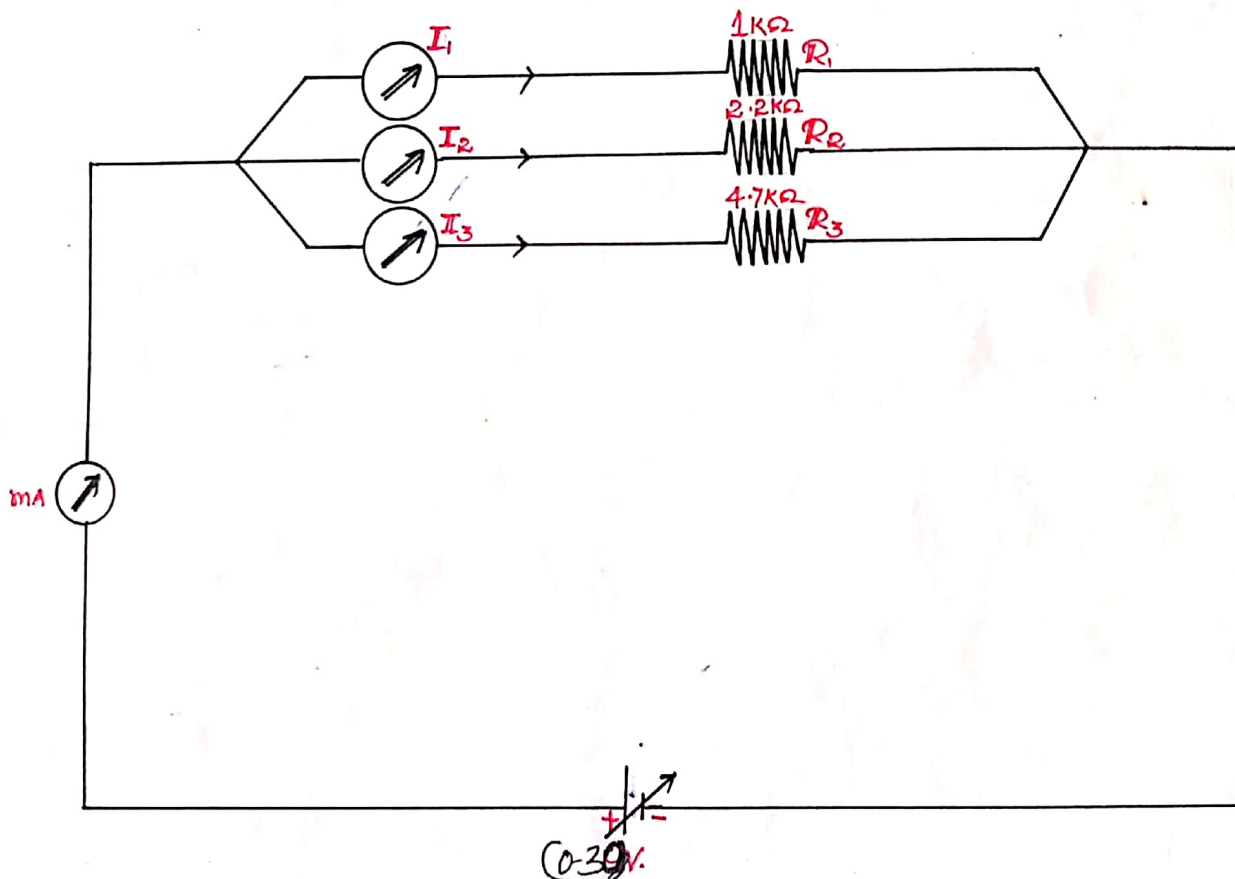1. Same voltage acts across all parts of circuits.
2. Different resistors have there indivisual current.
3. Branch current are additive.
4. Conductance are additive.
5. Power are additive.





$R_1 \rightarrow 1k\Omega$ ,  $R_2 \rightarrow 2.2k\Omega$ ,  $R_3 \rightarrow 4.7k\Omega$ ,  $V = 0-30V$

Ckt. Dia. of Parallel Resistance

## Circuit Diagram :-

## Procedure :-

1. Connect the ammeter, Voltmeter & resistor to the source by using patch cord as per the circuit diagram.
2. Check one's more the connection of parameter as per the circuit diagram.
3. Then switch on the supply.
4. Measure the total voltage V & Current I.
5. Calculate the value of R equivalent as  $R_{eq} = V/I$
6. Measure  $I_1, I_2$  &  $I_3$  across the resistor  $R_1, R_2$  &  $R_3$  respectively.
7. Calculate the value of  $R_1, R_2$  &  $R_3$  as  $R_1 = V/I_1, R_2 = V/I_2, R_3 = V/I_3$ . Find the  $1/R_{eq'}$  which is equal to  $1/R_1 + 1/R_2 + 1/R_3$ . Then find the difference between  $R_{eq}$  &  $R_{eq'}$ .

## Tabulation :-

Sl. no	Voltage in Volt	Current in mA	$R_{eq} = V/I$ in K ohm	$I_1$ Amp	$I_2$ Amp	$I_3$ Amp	$R_1 = V/I_1$ in K ohm	$R_2 = V/I_2$ in K ohm	$R_3 = V/I_3$ in K ohm	$1/R_{eq'} = 1/R_1 + 1/R_2 + 1/R_3$ in K ohm	$R_{eq'} = 1/(1/R_{eq'})$ in Kohm	Difference $R_{eq}$ & $R_{eq'}$

**Conclusion :-** From the above experiment we observed the laws of resistance in parallel is satisfied.

## **AIM OF THE EXPERIMENT :-**

Verification of Superposition Theorem.

## **APPARATUS REQUIRED :-**

1. C.T. Trainer Kit.
2. Patch Cord.

## **THEORY :-**

Superposition theorem states that , if there are a number of ~~there of~~ emfs acting simultaneously in any linear bilateral network, then each emf acts independently of the others i.e if the other emf acts independently of the others. i.e as the other emfs didn't exist. The value of current in any conductor is the algebraic sum of the currents due to each emf. Similarly voltage across any conductor is the algebraic sum of the voltages which each emf would have produced which acting singly.

Superposition theorem applicable only to linear networks where current is linearly related to voltage as per ohm's law.

## **EXPLANATION :-**

The theorem states that, in a network of linear resistances containing more than one source of emf or generator the current which flows at any point is the sum of all current which would flow at that point in each generator were considered separately and all the other generator replaced for the time being by resistances equal to there internal resistances.

$i_1, i_2, i_3$  &  $i$  represent the value of currents which are due to simultaneous action of the two sources of emf in the network.

$$i = i_1 + i_2 + i_3$$



## Circuit Diagram :-

Fig-1

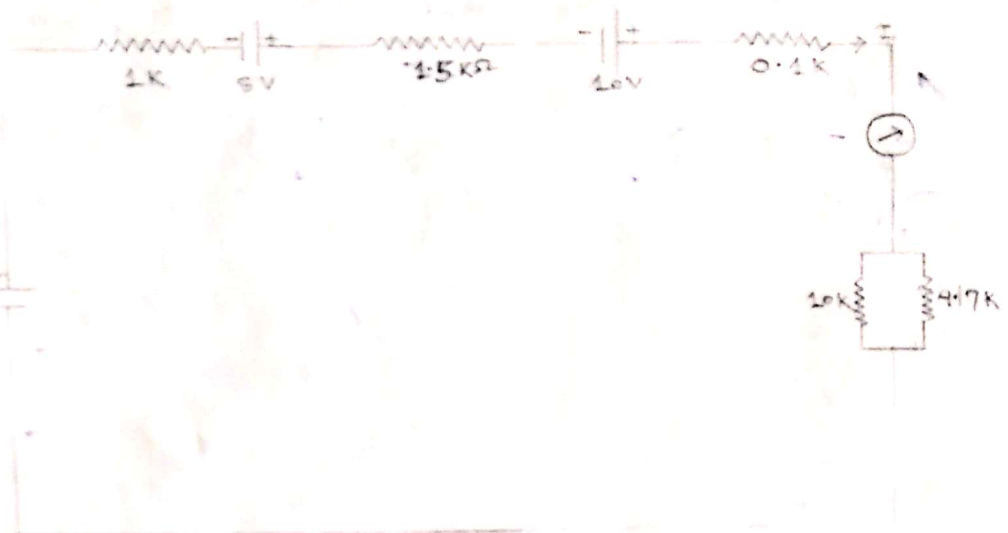


Fig-2

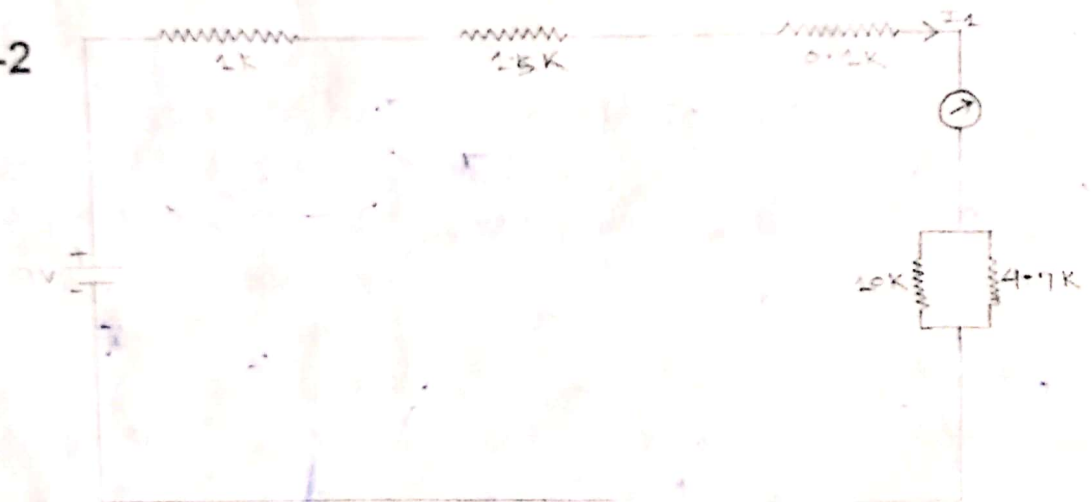


Fig-3


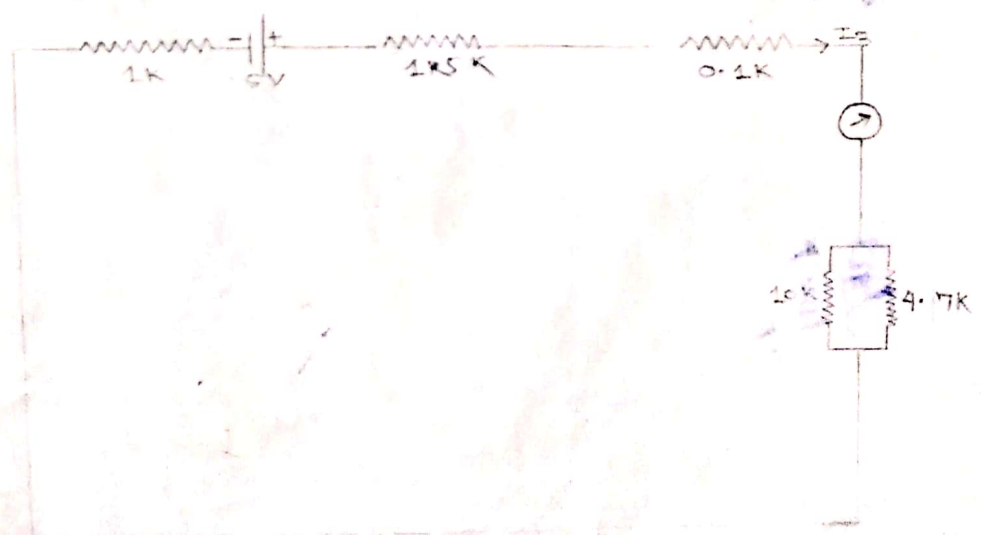


Fig - 4

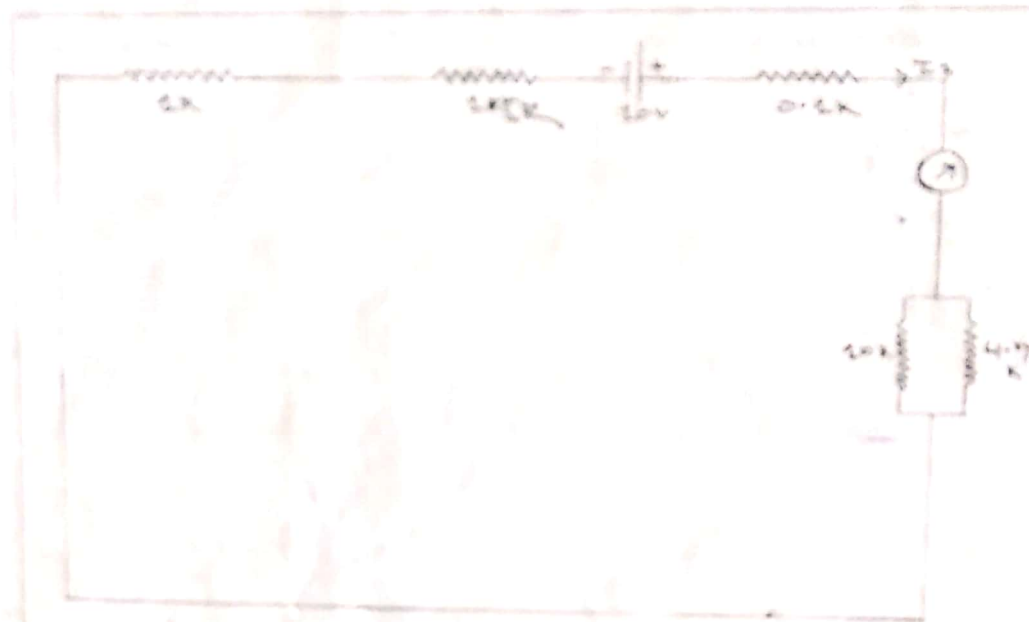

**PROCEDURE :-**

1. Connect the ammeter, Voltmeter & resistor to the source by using patch cord as per the circuit diagram.
2. Check one's more the connection of parameter.
3. Then switch on the supply.
4. Measure the total current  $i, i_1, i_2$  &  $i_3$ .
5. If there is more than one source, then measure the  $i_1, i_2$  &  $i_3$  one.
6. Consider all the sources as one source as one by one source as shows in circuit diagram and short the other sources.
7. Then calculate the  $i_1, i_2$  &  $i_3$  and find the difference between  $i$  &  $i'$  is equal to  $i' = i_1 + i_2 + i_3$

### TABULATION :-

SL NO	CURRENT (i) IN MA	CURRENT (i1) IN MA	CURRENT (i2) IN MA	CURRENT (i3) IN MA	$i' = i1+i2+i3$ MA	DIFF betn i & i1
1.						
2.						
3.						
4.						
5.						
6.						
7.						
8.						

### CONCLUSION TABULATION :-

From the above experiment we get a brief knowledge about the Superposition Theorem.

\*\*\*



## **Aim of the experiment :-**

Verification of Thevenin's theorem.

## **Apparatus Required :-**

1. Patch Cord
2. C.T. trainer board.


## **Theory :-**

Thevenin's theorem stated as, current flowing through a load resistance  $R_L$  across any two terminal of a linear, active, bilateral network is given by  $V_{oc}/R_i + R_L$  Where  $V_{oc}$  is the open circuit voltage (Voltage across two terminal when  $R_L$  is removed) and  $R_i$  is the internal resistance of network as viewed back into the open circuited network from terminals will all energy sources removed and replaced by their internal resistance (if any).

Calculate the Thevenin's Circuit :-

1. Temporarily remove the resistance as  $R_L$  whose current.
2. Find the open circuit voltage which appears across the two terminals from where resistance has been removed. It is also known as Thevenin's voltage.
3. Compute the resistance of whole network as looked into these two terminals after removed the all sources leaving behind their internal resistance & current sources has been replaced by open circuit i.e infinite resistance. It is also called Thevenin's resistance  $R_{th}$  or  $R_i$ .
4. Replace the entire network by a single Thevenin source whose voltage is  $V_{th}$  or  $V_{oc}$  and whose terminal resistance  $R_{th}$  or  $R_i$ .
5. Connect  $R_L$  back to its terminals from where it previously removed.
6. Calculate the current flowing through  $R_L$  by using the equation.  
$$I = V_{th}/(R_{th} + R_L) \text{ or } I = V_{oc}/(R_i + R_L)$$

# **Circuit Diagram :-**

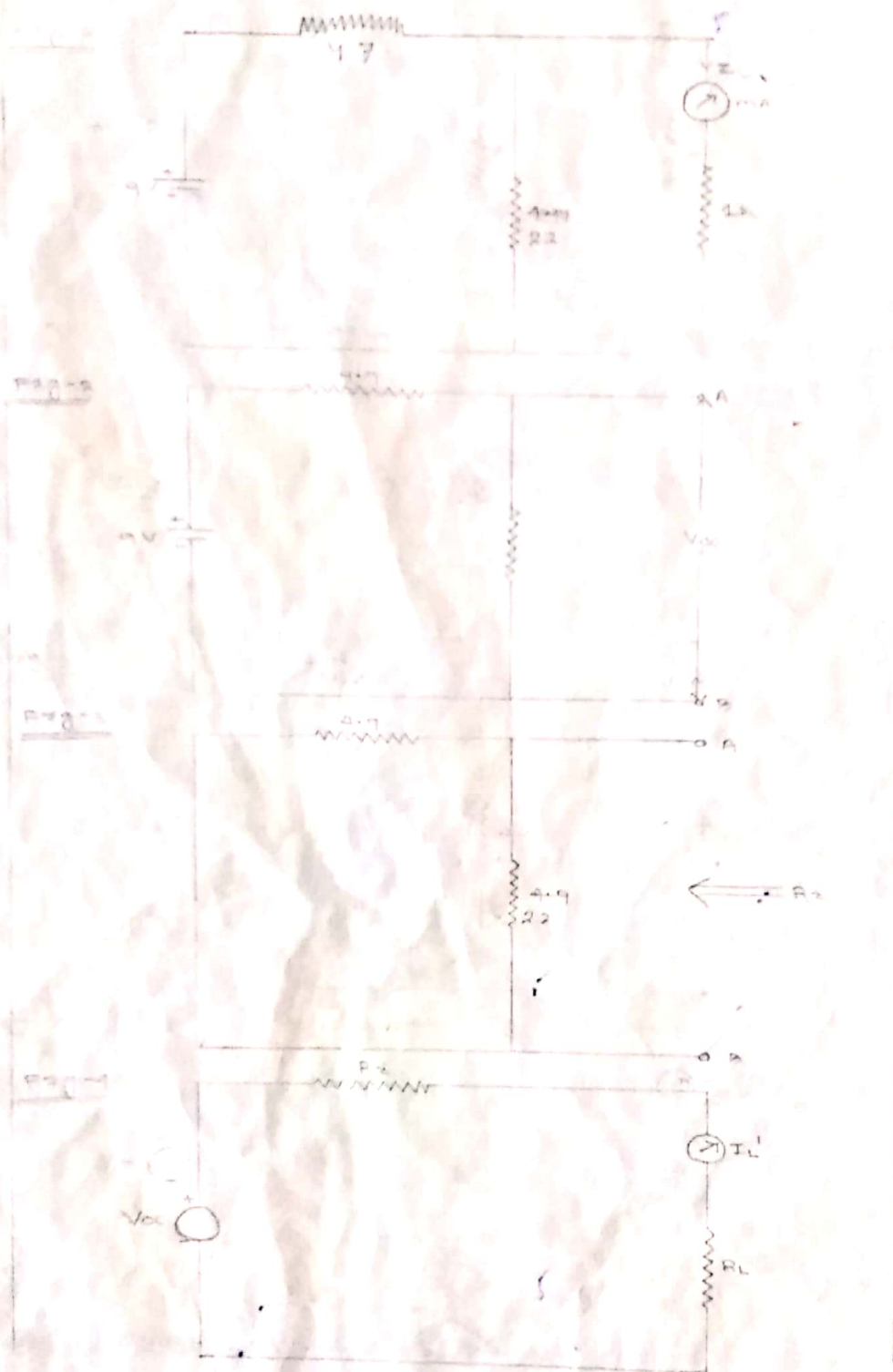

## Procedure :-

1. Connect the ammeter, voltmeter and resistor to the source by using patch cord as per the circuit diagram.
2. Check ones more the connections of the parameter as per the circuit diagram.
3. Then switch on the supply.
4. Measure the total current  $i$ .
5. If there is more than one source , the measure  $i_1'$ ,  $i_1''$ ,  $i_1'''$  are by one.
6. Considered all the sources as one source shows in circuit diagram & short the voltage sources & in current source open the circuit.
7. Then calculate the  $V_{oc}$  & internal resistance  $R_i$  such as equivalent resistances.
8. After that calculate  $i_L$  &  $i_L'$  and their differences.

## Tabulation :-

Sl.no	Voltage in Volt	Current $i_L$ in mA	Voc In Volt	Internal resistance $R_i$ in ohms	$i_L'$ in m.A	Difference $i_L$ & $i_L'$

## Conclusion :-

From the above experiment we get knowledge about the Thevenin's theorem.

\*\*\*



## AIM OF THE EXPERIMENT :-

Verification of the maximum power Transform theorem.

## APPARATUS REQUIRED :-

- (1 ) Patch Cord
- (2) C.T. Trainer Kit.

## THEORY :-

Maximum Power transform theorem states that, A resistive load abstract maximum power from a network when the load resistance is equal to the resistance of network as views from the output terminals, with all energy sources removed leaving behind their internal resistances.

A load resistance  $R_L$  is connected across the two terminal of the network which consist of a generator emf  $E$  & internal resistance  $R_g$  & a series resistance  $R$  which infact, represents the lumped resistance of the connecting wires.

Let  $R_i = R_g + R =$  internal resistance of network.

According to this theorem,  $R_L$  will abstract maximum power from the network when  $R_L = R_i$


Circuit current =  $I$

Power consumed by the load is  $P = i^2 R_L$

## CIRCUIT DIAGRAM :-



## CRT.DIA. MAXIMUM POWER THEOREM.

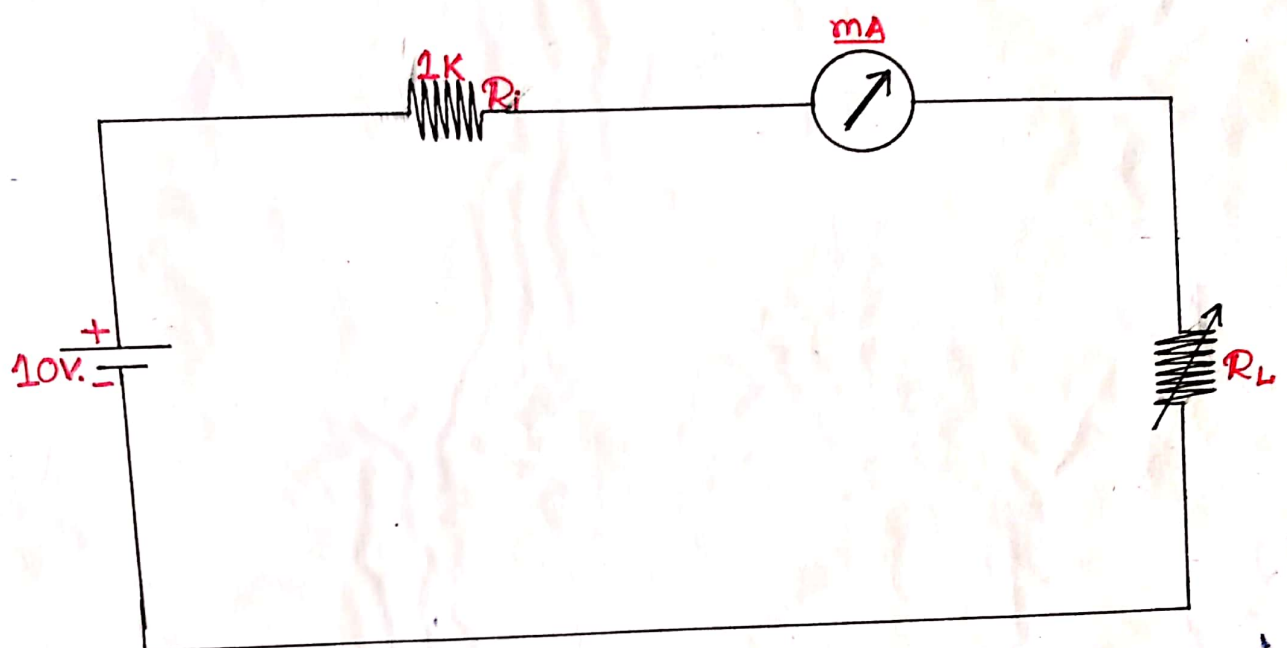

### PROCEDURE :-

- (1) Connect the ammeter, Voltmeter & Resistor to the source by using patch cord as per the circuit diagram.
- (2) Check one's more the connection of parameter as per the circuit diagram.
- (3) Then switch on the supply.
- (4) Measure the current "i" for different value of load register RL.
- (5) Calculate the power for different value of current i and different load register RL & maximum power P max of the circuit.

### TABULATION :-

Sl. No	Resistance (R) in Kohm	Load Resistance RL in Kohm	Current (i) in m.A.	Power $P = i^2 R_L$ in mW
1.				
2.				
3.				
4.				
5.				
6.				
7.				
8.				
9.				

### CONCLUSION :-

From the above experiment we get knowledge about maximum power transfer theorem.

\*\*\*\*\*



## **Aim of the Experiment :**

Verification of Norton's theorem.

## **Apparatus Required :**

1. CT trainer board.
2. Patch Cord.

## **Theory :**

Norton's theorem states that, any two terminal active network containing voltage sources & resistances when viewed from its output terminal, is equivalent to a constant current source and a parallel resistance. The constant current is equal to the current which would flow in a short circuit placed across the terminal and parallel resistance is the resistance of the network when viewed from these open circuited terminals after all voltage & current sources have been removed and replaced by their internal resistances.

The voltage between any two points in a network is equal to  $I_{sc} \cdot R_i$  where  $I_{sc}$  is the short circuit current and  $R_i$  is the internal resistance of the network as viewed from these terminal with all voltage sources being replaced by their internal resistances (if any) and current sources replaced by open circuit.

## **Calculate the Norton's circuit :-**

1. Remove the resistance (if any) given the two across the two given terminals and put a short circuit across between these two points.
2. Then compute the short circuit current  $I_{sc}$ .
3. Remove all voltage sources but retain their internal resistances (if any). Similarly remove all current sources & replace them by open circuits i.e. by infinite resistances.
4. Then find  $R_i$  &  $R_N$  of the network as looked into from the given terminals.



- 5. The current sources ( $I_{sc}$ ) joined in parallel across  $R_i$  between the two terminals gives Norton's equivalent circuit.

### Circuit Diagram :-

CIRCUIT 1 Diagram  
Fig-1

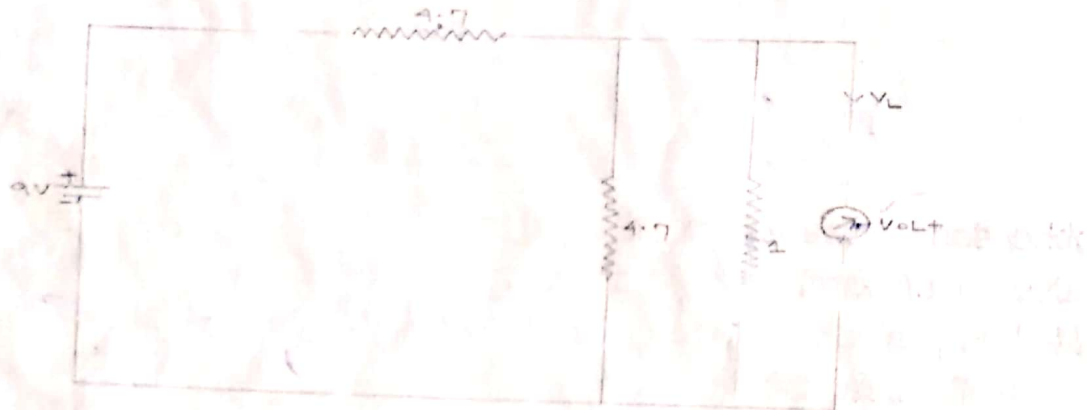


Fig-2



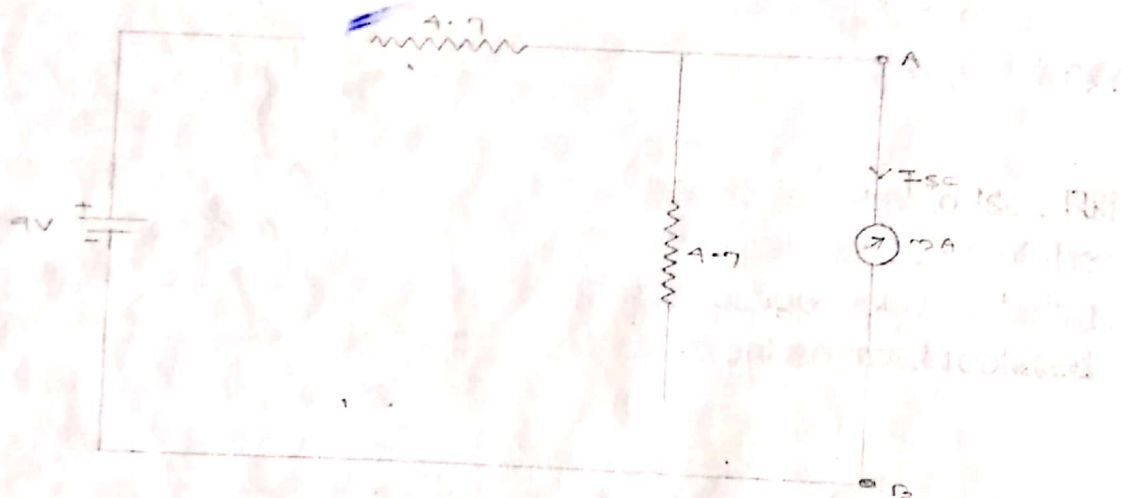


Fig-3

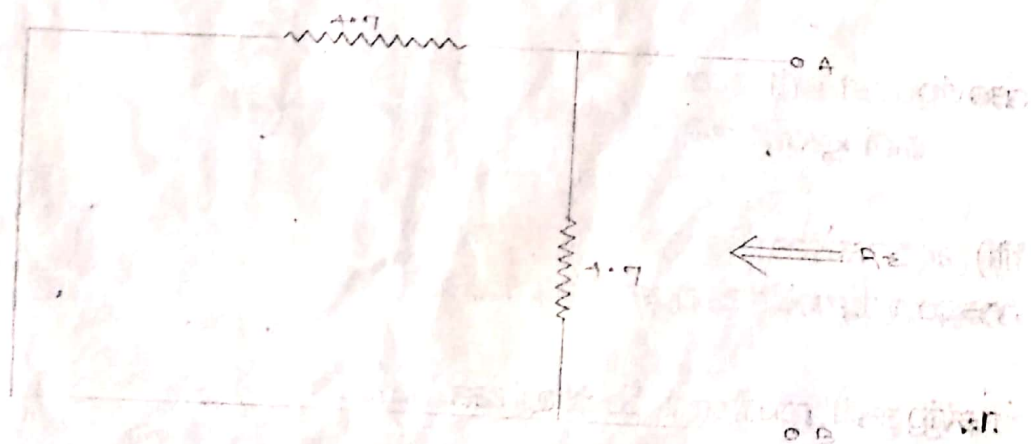

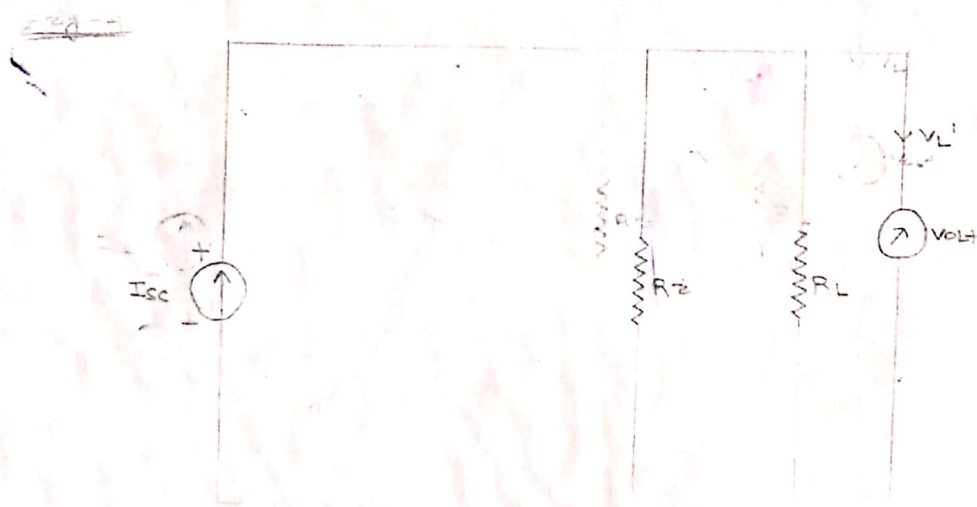

### Procedure :-

1. Connect the ammeter, Voltmeter and resistance to the source by using patch cord as per circuit diagram.
2. Checked ones more the parameter connections as per as circuit diagram.
3. Then switch on the supply.
4. If there is more than one source then measure  $i_1', i_1'', i_1'''$  one by one.
5. Measure the total voltage  $V_L$ .
6. Consider all the sources as one source shows in circuit diagrams & short the voltage sources & in current source open the circuit.
7. Then calculate the  $i_{sc}$  & internal resistance  $R_i$  such as equivalent resistance.
8. After calculated the  $V_L$  &  $V_L'$  then find the difference between them.

### Tabulation :-

Sl.no	Voltage in Volt	$V_L$ in Volt	$I_{sc}$ in m.A	Internal Resistance $R_i$ in Ohm	Load Resistance $R_L$ in Ohms	$V_L'$ in Volt	Difference $V_L - V_L'$

### Conclusion :-

From the above experiment we get a brief knowledge about Norton's theorem.

## AIM OF THE EXPERIMENT :

Fourier series analysis of non-sinusoidal waveform.

Aim of the experiment:-

### FOURIER SERIES

To study the low pass filter and its implementation.

Apparatus required:-

1. low pass filter trainer kit
2. CRO
3. Patch cord

Theory:-

A low pass filter is a circuit which allow low frequency of the signal to pass and reject all the other frequency. It is evident from fig. that with increase in frequency of the signal at input side shunt capacity reactance decreases. This will allow more current to be returning back to the source through the impedance path. At the high frequency, the entire input current returns to the source through shunt branch which become practically a short circuit link at this frequency.

Thus it is evident that the low pass section can only allow passage of signal through it, till signal frequency is at low magnitude. At higher frequency in inductive reactance in the series are also increases to a very high value rendering the blockage of the input signal in practice LPF operation is said to be satisfactory for increasing frequency till the gain is 0.707.

cut-off frequency is given by :-  $F_c = 1/\pi\sqrt{LC}$

Design impedance  $R_0 = \sqrt{L/C}$

Impedance across inductor  $X_L = \omega L$

Impedance across capacitor  $X_C = 1/\omega C$

Which can be

For low frequency  $\omega L \ll 1/\omega C$  so  $V_{in} \sim V_{out}$

For high frequency  $\omega L \gg 1/\omega C$  so  $V_{out} \sim 0$

Since output voltage signal is equal to the signal strength across capacitor. Hence in above ckt the signal will only arise across capacitor at low frequency. Hence this type of filter allows a signal to appear across capacitor from low value of frequency (F), it will attenuate the signal across capacitor for high value of frequency. Hence it acts as LPF.

Procedure:-


Procedure:

We have to connect the circuit as per the circuit diagram then increase the input frequency and determine output from CRO




$$\int_0^{\pi} \sin n \omega t \cdot \sin n \omega t \cdot dt = \dots (n, m = n)$$

CIRCUIT DIAGRAM:-

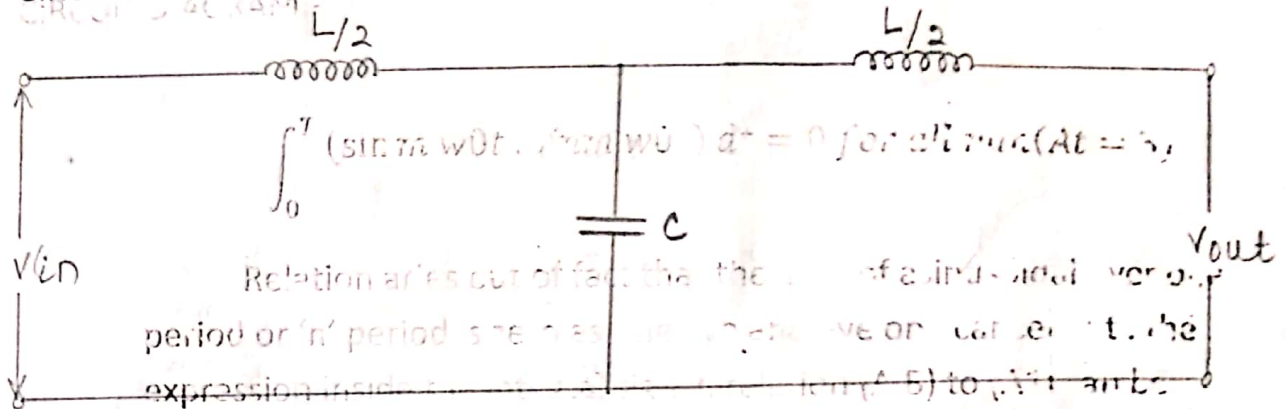

Relation arises out of fact that the ... of a sinusoidal wave ... period or 'n' period ... the expression inside ... to ...

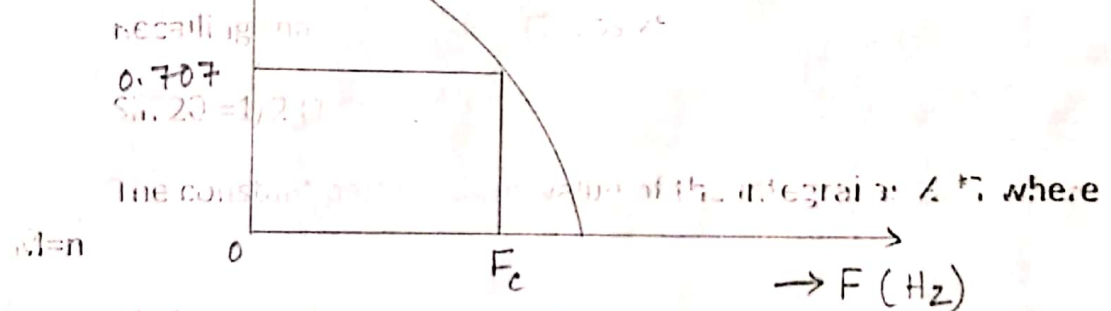expressed ... the integral becomes zero for the same ... expression is when  $m=n$  eqn.



Tabulation:-

SL. no.	$V_0$ (in volt)	$T$	$F=1/T$	$\omega=2\pi f$
	0			

Conclusion:-

From the above experiment, we study about the LPF and plot a graph between  $V_0$  and  $F_0$ .

CONCLUSION

From the above experiment we studied about fourier series analysis by sinusoidal waveform.



**Aim of the experiment:-**

To study the bandpass filter and its implementation.

**Apparatus required:-**

1. band pass filter trainer kit
2. CRO
3. Patch chord

**Theory:-**

A band pass filter is a circuit which pass a certain range of frequency and rejects all other frequencies. This frequency lies between the lower cut off frequency and upper cut off frequency in RLC type band pass filter.

$$V_0 = V_i \cdot R / \sqrt{R^2 + (X_L - X_C)^2}$$
$$= V_i \cdot R / \sqrt{R^2 + (2\pi fL - 1/2\pi fc)^2}$$

Here  $R = [(R_f + R_L) / R_f \cdot R_L] \cdot L$

Where

$R_f$  = Filter resistance

$R_L$  = Load resistance

$V_i$  = input voltage

$V_0$  = output voltage

From the frequency of series resonance, varies in frequency is given by,

$$F_0 = 1/2\pi\sqrt{LC} \text{ Hz}$$

The Q factor is given by

$$Q = \omega_0 L / R$$


$$\text{Bandwidth} = F_0 / Q \text{ Hz}$$

$$F_1 = F_2 = B.W / 2 \text{ HZ}$$

$$F_2 = F_0 + B.W / 2 \text{ HZ}$$

Where  $f_1$  and  $f_2$  are lower and upper cut off frequency.

CIRCUIT DIAGRAM:-

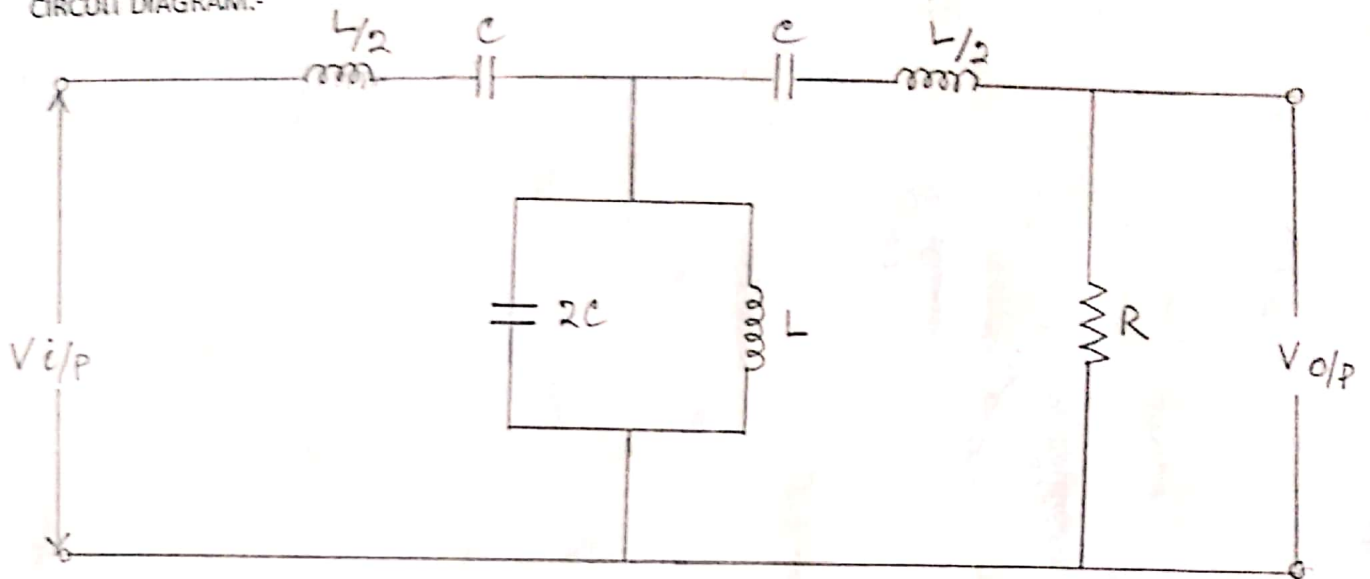

PROCEDURE:-

We have to connect the circuit as per the circuit diagram then determine the maximum resonant frequency. Determine the upper cutoff frequency  $f_1$  and by determining  $f_1$  the lower cutoff frequency and the range between  $f_1$  &  $f_2$  is known as bandwidth which is determined by band pass filter.

Tabulation:-

SL. no.	T(ms)	F(KHZ)	$V_o(mv)$	$\omega=2\pi f(KHZ)$

Conclusion:-

From the above experiment, we study about the band pass filter circuit which flows the signal of certain ranges and reject all other.

## AIM OF THE EXPERIMENT :-

Determine resonant frequency of R-L-C series circuit.  
(Bandwidth, Q-factor)

## APPARATUS REQUIRED

- 1) Power Supply
- 2) Function Generator.
- 3) CRO
- 4) Series Resonance kit
- 5) connecting leads.
- 6) Multi-meter.

## THEORY :-

The circuit is said to be in resonance if the current is in phase with the applied voltage. Thus a Resonance, the equivalent complex impedance of the circuit consists of only resistance (R). Since  $V$  &  $I$  are in phase, the power factor of resonant ckt is unity.

The Total impedance for the series R-L-C ckt is,

$$\begin{aligned} Z &= R + j(X_L - X_C) = R + j(\omega L - \frac{1}{\omega C}) \\ &= R + jX \end{aligned}$$

The ckt. is in resonance when  $X = 0$ , i.e.  $Z = R$

Series Resonance occurs

$$\text{when } X_L = X_C$$


$$\text{i.e. } \omega L = \frac{1}{\omega C}$$

$$\cancel{2\pi f_r L} = \frac{1}{\cancel{2\pi f_r C}} = 2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$\Rightarrow f_r^2 = \frac{1}{4\pi^2 LC}$$

$$\Rightarrow f_r = \frac{1}{2\pi} \sqrt{LC}$$

### CIRCUIT DIAGRAM

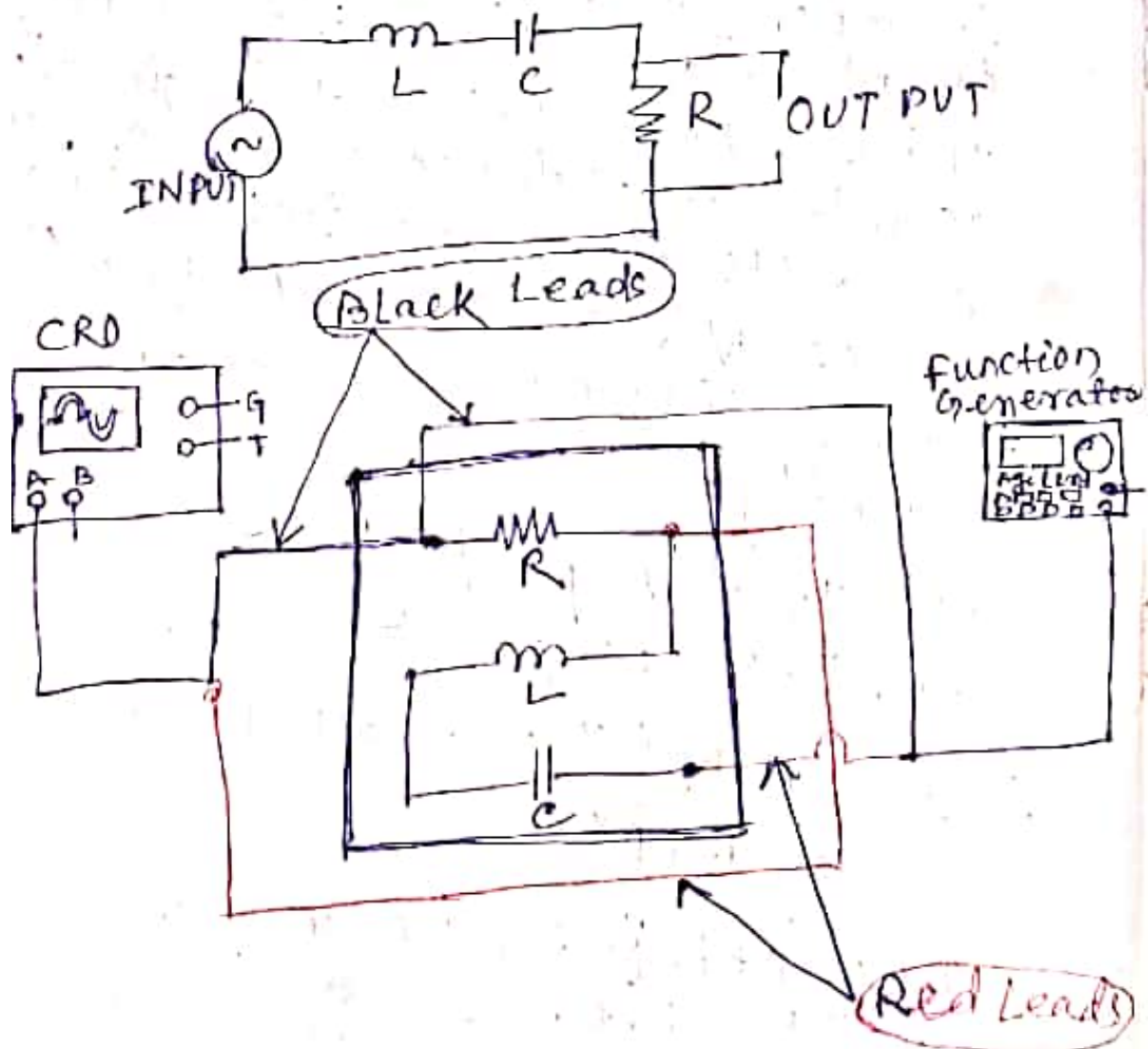



## SIMPLE CALCULATION

$$F_r = V_{\max}$$

$$\text{Band width} = (f_2 - f_1) \text{ KHz}$$

$$f_2 - f_1 = 0.707 V_{\max}$$


$$Q = \frac{F_r}{\text{Band width}}$$

## TABULATION Table-1

Table-1 ckt. Parameters	calculated Resonant frequency	
R = _____	Experimental Resonant frequency	
L = _____		
C = _____	% Difference	

TABLE-2	
frequency (Hz)	Peak to peak voltage
50	
100	
...	
Resonant frequency	

Graph

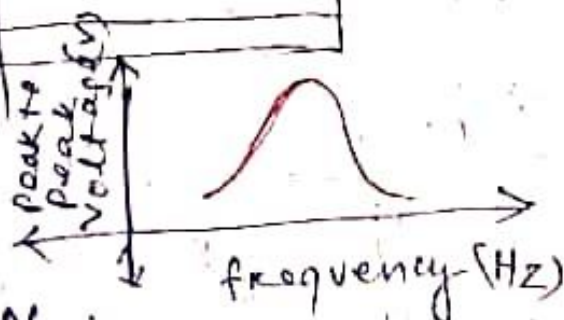

## CONCLUSION :-

The resonance frequency, Bandwidth and Q-factor of R-L-C Series circuit has been calculated.

### AIM OF THE EXPERIMENT:-

To study and plot the transient response of RC circuit.

### APPARATUS REQUIRED:-

- 1) Power supply
- 2) Circuit Board kit.
- 3) CRO
- 4) Function Generator.
- 5) Connecting leads.

### THEORY:-

Let initially the switch 'K' is at position '1'. When it is moved to position '2' then apply KVL.

$$\frac{1}{C} \int i dt + Ri = V.$$

Now differentiating w.r.t 't'.

$$\frac{1}{C} i + R \frac{di}{dt} = 0.$$

$$\Rightarrow R \frac{di}{dt} = -\frac{1}{C} i$$

$$\Rightarrow \frac{di}{i} = -\frac{1}{RC} dt$$

Integrating w.r.t 'i' & then taking log on both side.



Samsung Triple Camera

Shot with my Galaxy M30s

This is general soln of RLckt  
if the value of  $C_2$  is calculated  
then the result is known as  
particular soln.

Just before switching at  $t=0$

$$i(0) = \frac{V}{R}$$

putting this in equ<sup>n</sup> ①

$$i(0) = C_2 \text{ @}$$


$$\Rightarrow \frac{V}{R} = C_2$$

$$\Rightarrow C_2 = \frac{V}{R}$$

$\therefore$  Particular solution is

$$i = \frac{V}{R} e^{-\frac{Rt}{L}}$$

### CIRCUIT DIAGRAM

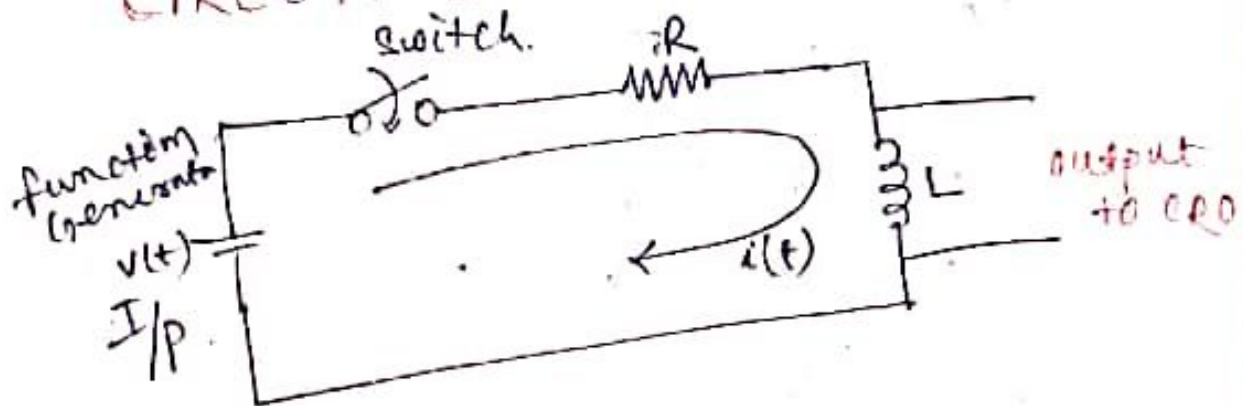

### PROCEDURE:-

- 1) connect the circuit according to the figure and switch on the supply.





2) feed square wave from the function generator to the I/p terminal of the ckt.

3) connect the CRO to the o/p terminal and note down the op wave.

4) Draw the I/p and o/p wave on the graph paper.

5) switch off the power supply after taking the wave.

GRAPH:-

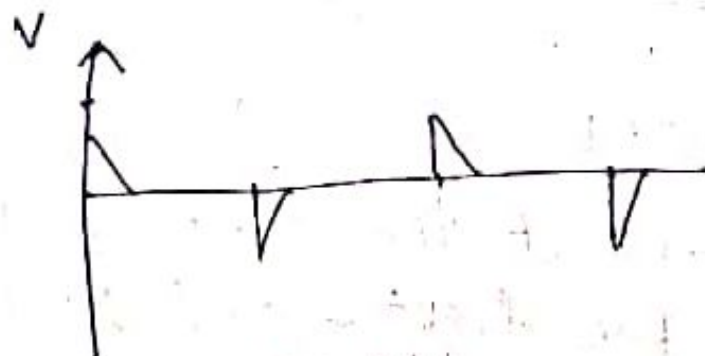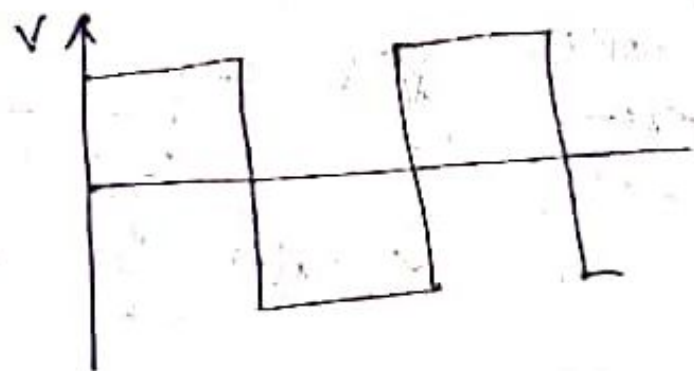

CONCLUSION:-

Transient response of RL ckt has been studied and the results obtained are shown on the graph.



## AIM OF THE EXPERIMENT:-

To study and plot the transient response of RL circuit.

## APPARATUS REQUIRED:-

- 1) Power supply
- 2) Circuit Board kit
- 3) CRO
- 4) function Generator.
- 5) connecting leads.

## THEORY:-

Let switch 'K' be at position 1. When it is switch to 2 then

$$L \frac{di}{dt} + Ri = 0$$

$$\Rightarrow L \frac{di}{dt} = - Ri$$

$$\Rightarrow \frac{di}{dt} = - \frac{R}{L} i$$

$$\Rightarrow \frac{di}{i} = - \frac{R}{L} dt$$

Integrating & then taking log on both sides

$$\log i = - \frac{Rt}{L} + \log c \quad \text{where } c \text{ is const}$$

$$\Rightarrow i = c e^{-\frac{Rt}{L}} \quad \text{--- (1)}$$

$$\log i = -\frac{1}{RC} t + C_2$$

$$i = C_2 e^{-\frac{t}{RC}} \quad \text{--- ①}$$

on putting  $i = \frac{V}{R}$  in eqn ①  
we get

$$\frac{V}{R} = C_2 e^{-\frac{t}{RC}}$$

At  $t = 0$


$$\frac{V}{R} = C_2 e^0$$

$$\Rightarrow C_2 = \frac{V}{R}$$

putting the value of  $C_2$  in eqn ①

$$i = \frac{V}{R} e^{-\frac{t}{RC}}$$

CIRCUIT DIAGRAM:-

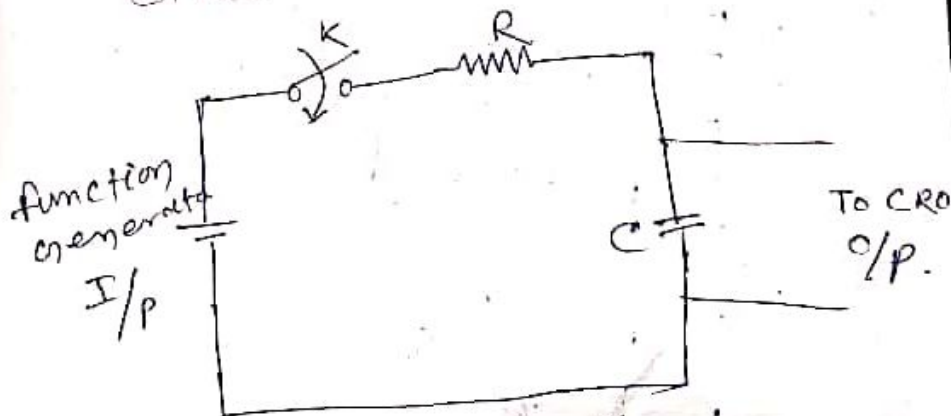



Samsung Triple Camera

Shot with my Galaxy M30s

### PROCEDURE:-

- 1) connect the ckt according to the figure & switch ON the supply.
- 2) feed square wave from function generator to the I/p terminal of the ckt.
- 3) connect the CRO to the o/p terminal & note down the o/p wave.
- 4) Draw the I/p and o/p wave on the graph paper.
- 5) Switch off the power supply after taking the wave.

### GRAPH:-

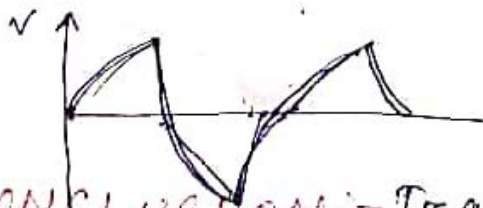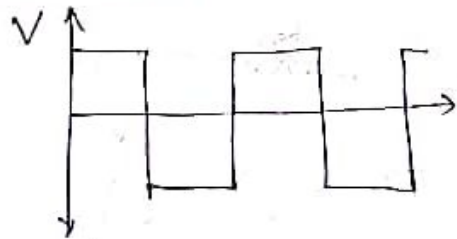

CONCLUSION:- Transient response of RC ckt has been studied and the result obtained are shown on the graph.



Samsung Triple Camera  
Shot with my Galaxy M30s